

***Project: Switched Capacitor Active Band-Pass Filter******Abstract***

The main objective of this design project is to help students to design and implement solutions for electrical engineering problems by making them familiarize with different types of electronic circuits consisting of several components such as ICs, MOSFETs, resistors and capacitors in order to know how to design, construct and test these circuits using the following two different methods. First of all, we use the Pspice programming to analyze and design several electronic circuits where in this project we use the Pspice programming in order to design and analyze the circuit in figure 1 as shown in pages 5 & 6. Second, we implement our electronic circuit for this project in the Electronics II Lab, and we verify our results as shown in the images taken from the oscilloscope. Ultimately, we apply what we have learned so far from the lectures in implementing and designing our circuit design for this project.

*Table of Contents*

**Abstract .....2**

**Table of Contents.....3**

**List of Figures .....4**

**PSPICE Simulations.....5**

**Part I Results.....7**

**Part II Results.....9**


**Conclusion .....14**

### *List of Figures*


<i>Fig. Number</i>	<i>Details</i>
<i>1</i>	<b>Operational Amplifier Circuit</b>
<i>2</i>	<b>Operational Amplifier Circuit with Switched Capacitor</b>
<i>3</i>	<b>The Second Order Band Pass Filter</b>
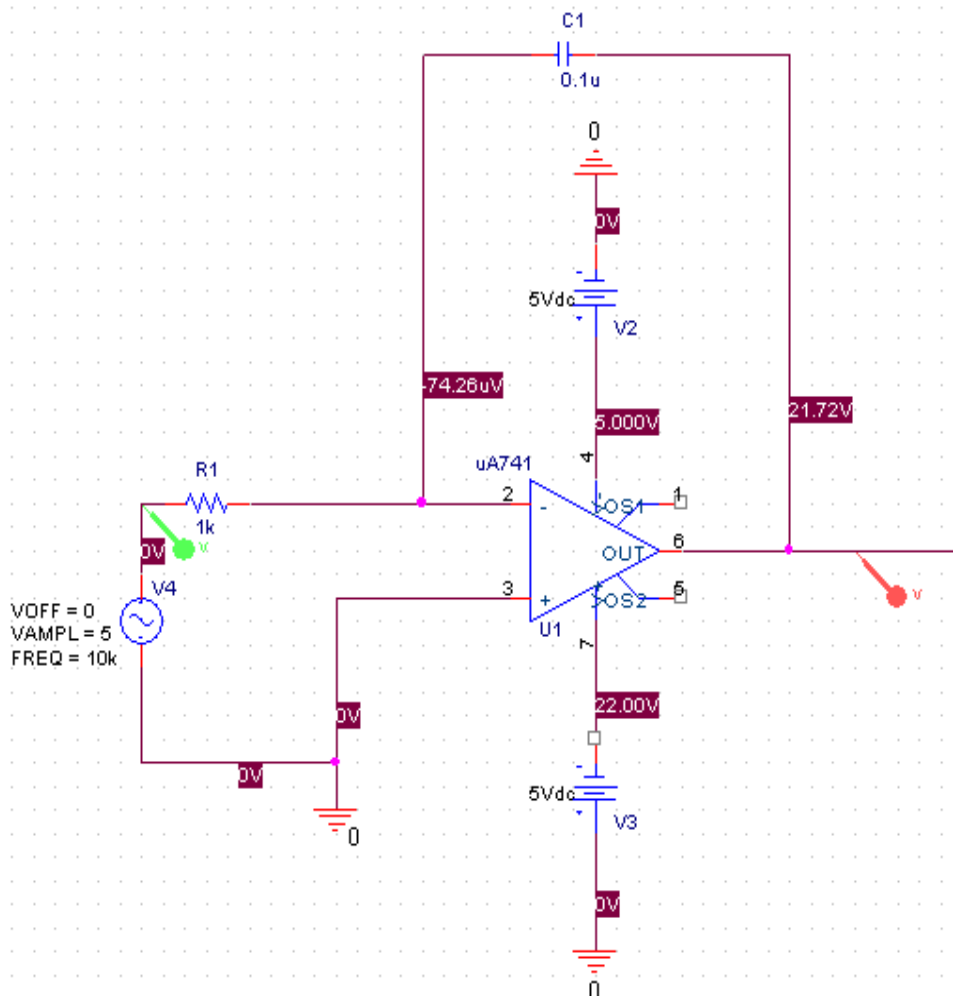
### Pspice Simulation:-

We simulate our electronic circuit design for figure 1 using the Pspice software as shown below in this page and the next page as well.




Ultimately, we got the following waveforms from the Pspice simulations as follows:

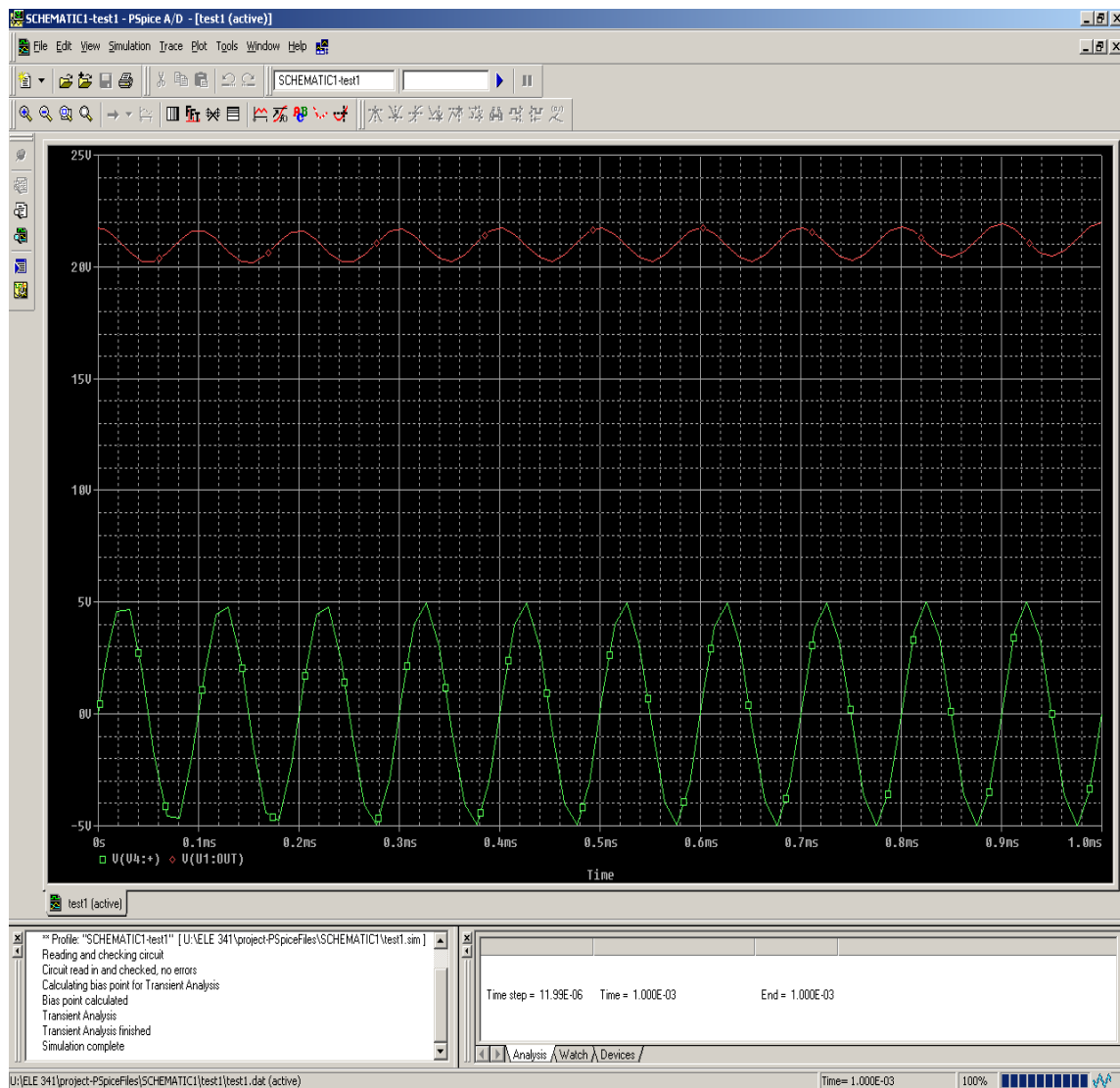

**Part I: Results**


First of all, we implement the circuit given below using  $R_1=1k\Omega$  and  $C_2=0.1\mu F$ .

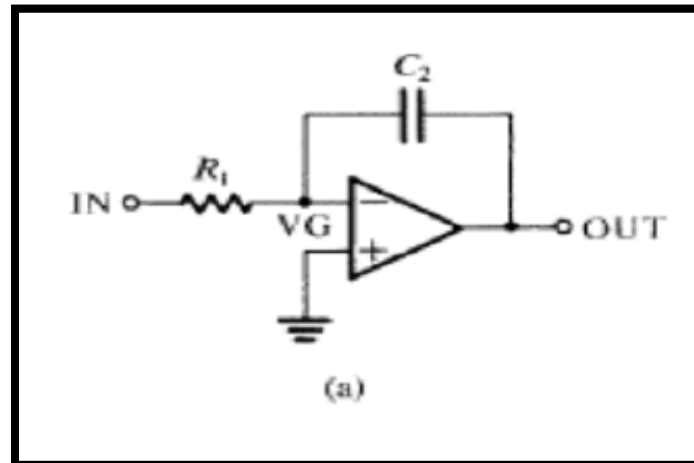

**Figure 1: Operational Amplifier Circuit**

Then, we measure the cutoff frequency for the above circuit which is equal to 400kHz.

Moreover, we implement the circuit given in the figure 2 below.

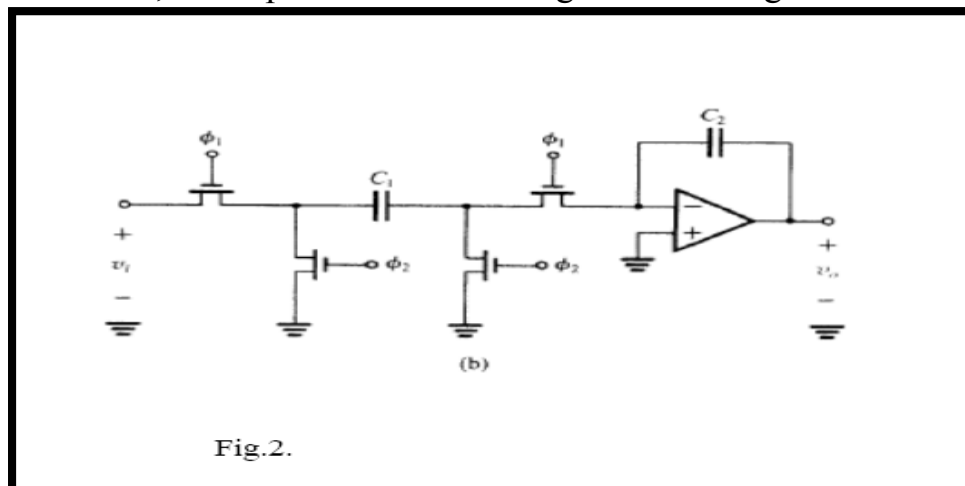

**Fig.2.**

**Figure 2: Operational Amplifier Circuit with Switched Capacitor**

*Then, we measure the cutoff frequency values for two cases:*

*Case 1: using the clock frequency  $\Phi_1 = 10\text{KHz}$ .*

*The cutoff frequency for case 1 is 172Hz*

*Case 2: using the clock frequency to 100 KHz*

*The cutoff frequency for case 2 is 421Hz*

### Comment on Results

Replacing the first resistor (R1) by the switch capacitor in the above figure 2 will change the cutoff frequency values where increasing the clock frequency value such as using 100kHz will increase the value of cutoff frequency from 172Hz to 421Hz in the ratio of about two times. Also, changing the clock frequency will change the cutoff frequency values as a result because the clock signals are out of the phase where the clock frequency =  $1/T_c$  such as if the clock frequency equals 10kHz, then the period will equal to  $1/10\text{kHz}=0.0001$  and by increasing the clock frequency to be equal to 100kHz, the period will equal to  $1/100\text{kHz}=0.00001$ . Ultimately, increasing the period  $T_c$ , the equivalent resistance will increase according to  $R_{eq}=T_c/C_1$ , and as a result the  $C_1$  will be decreasing. Therefore, the value of cutoff frequency will be increasing as the capacitor decreasing because the cutoff frequency is inversely proportional to the capacitor as follows:

$$\text{Cutoff frequency} = f = \frac{1}{2\pi\tau_p} \quad \text{where } \tau_p = R_{eq} * C.$$

## Part II: Results

In this part, we design and implement a second order band pass filter as given in Figure.3 below with  $f_0 = 10 \text{ kHz}$ ,  $Q = 20$  and unity center frequency gain. Moreover, we verify the frequency response of circuit given by Figure.3 using component values for our design. Furthermore, we replace resistor  $R_g$  by switched capacitor circuit in order to get the same pass band for the filter, and we verify the pass band and  $Q$  values by using clock frequency  $\Phi_1 = 200 \text{ kHz}$ .

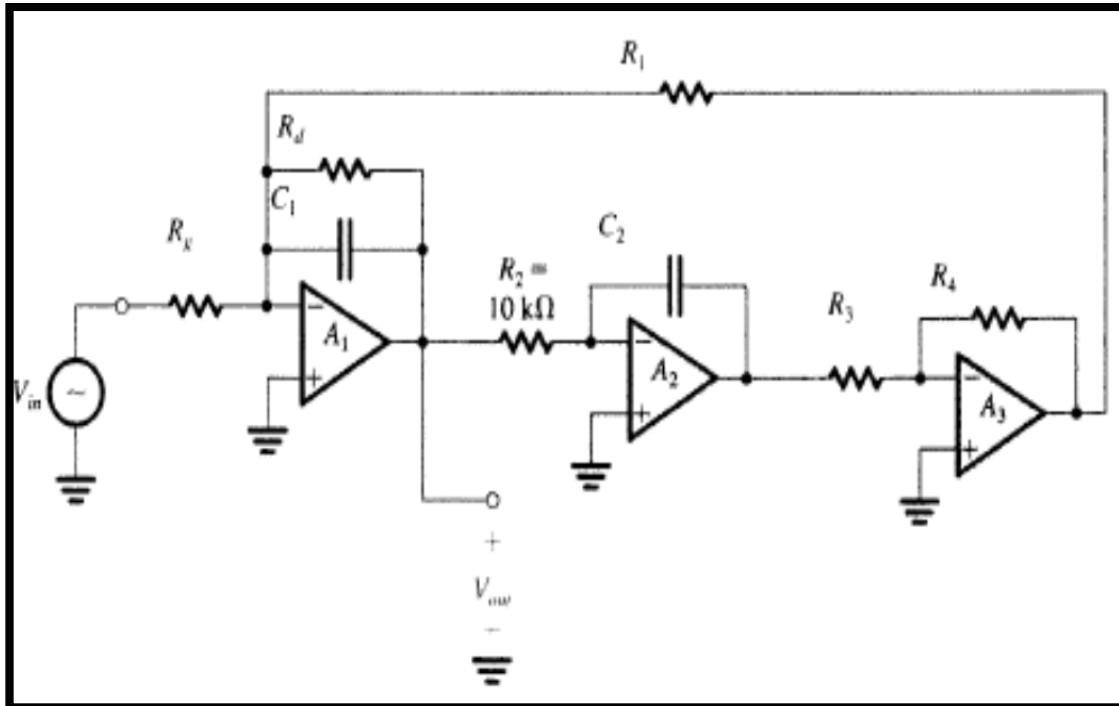


Figure 3: The Second Order Band Pass Filter

### Design Calculations

Let  $C_1 = 10 \text{ nF} = C_2$ .

$Q = 20 \rightarrow BW = f_0/Q = 10\text{K} / 20 = 500$

$R_g = 1/(2 * \pi * R * BW) = 31.8 \text{ k}\Omega$


$A_v (\text{max}) = R_g/R$  and  $A_v = 1$  (unity gain)  $\rightarrow R_g = R = 31.8 \text{ k}\Omega$

$f_0 = 1/(2 * \pi * C * \sqrt{R_2 * R_1})$ ,  $R_2 = 10\text{k} \Omega \rightarrow R_1 = 253 \Omega$


Let  $R_3 = R_4 = 1.2\text{k}\Omega$



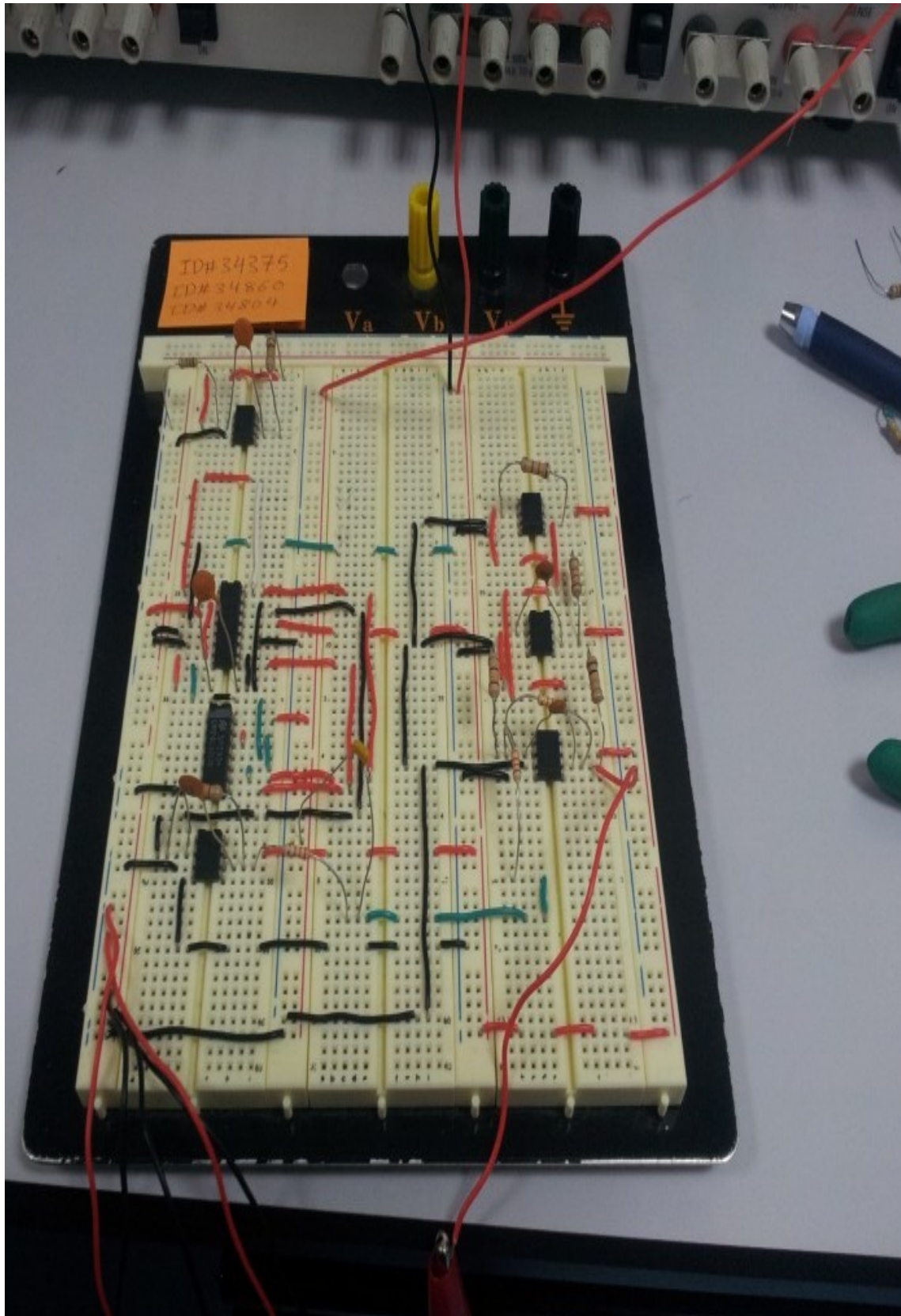
*Some images from our circuit implementation in the Electronics II Lab*




*Our Circuit Design*

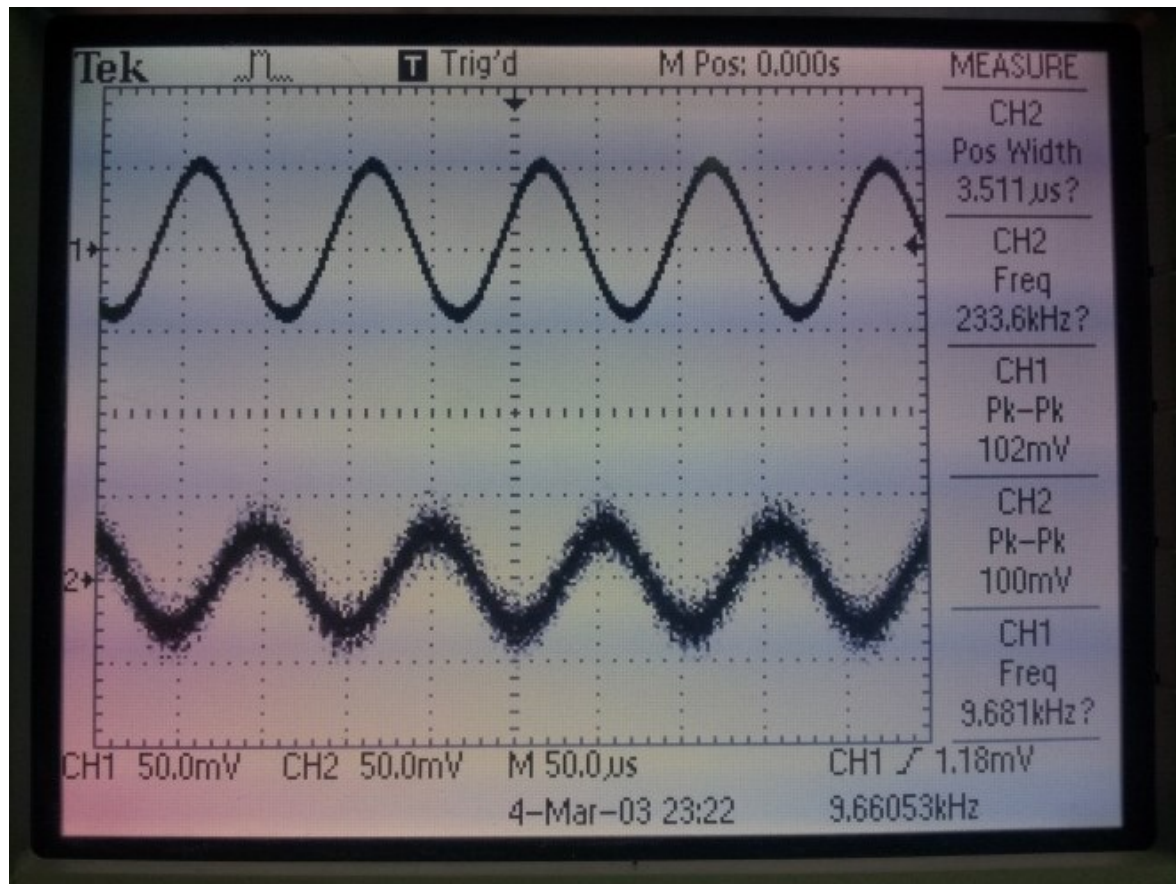


*Band Pass*

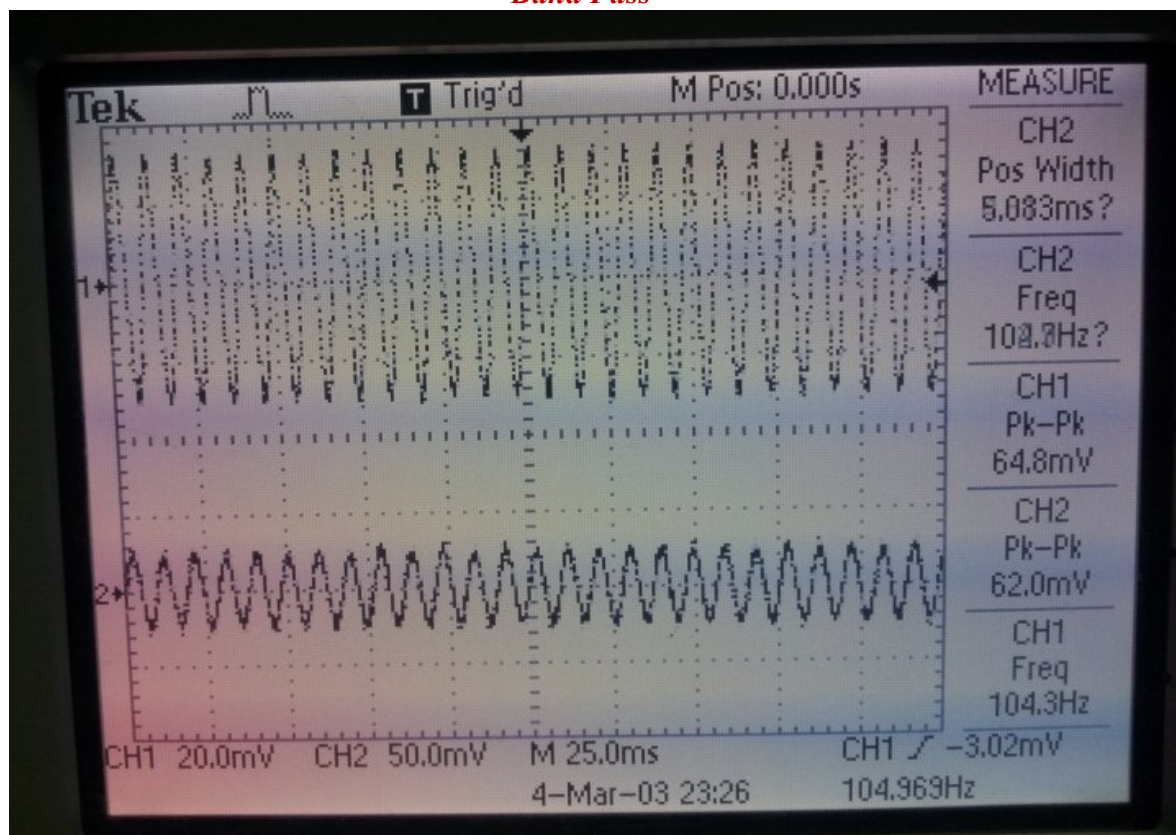


The Output after Switched Capacitor

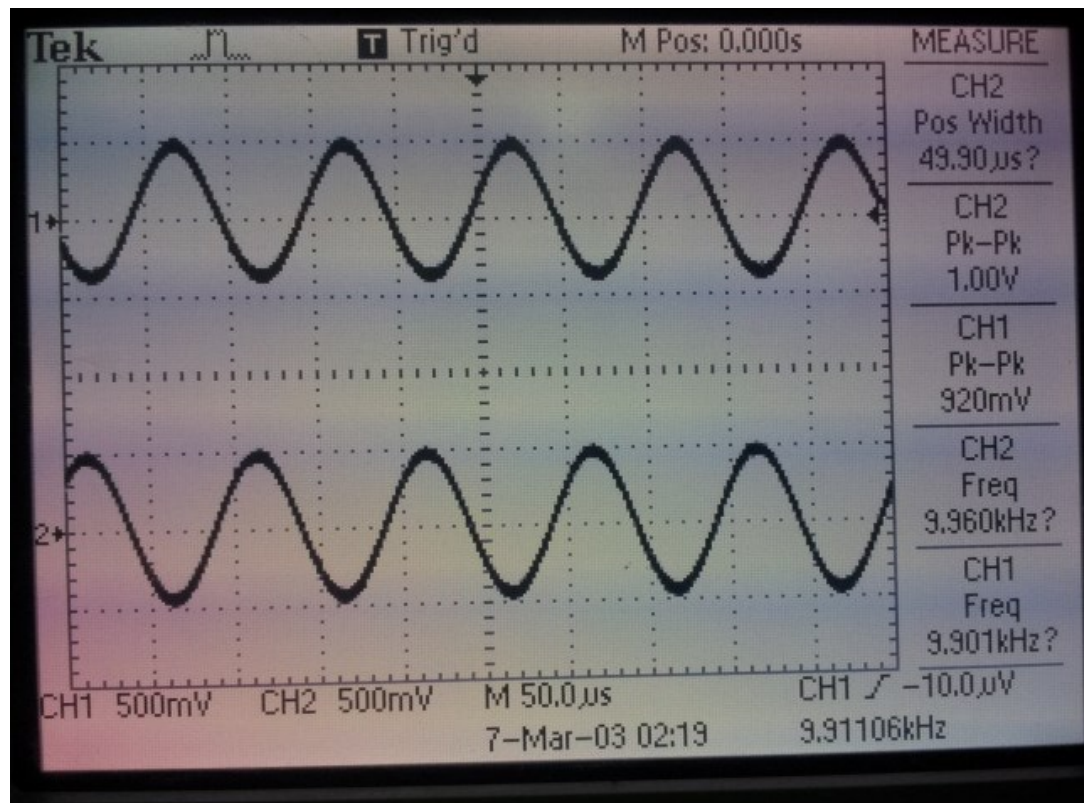

*Pass Band*

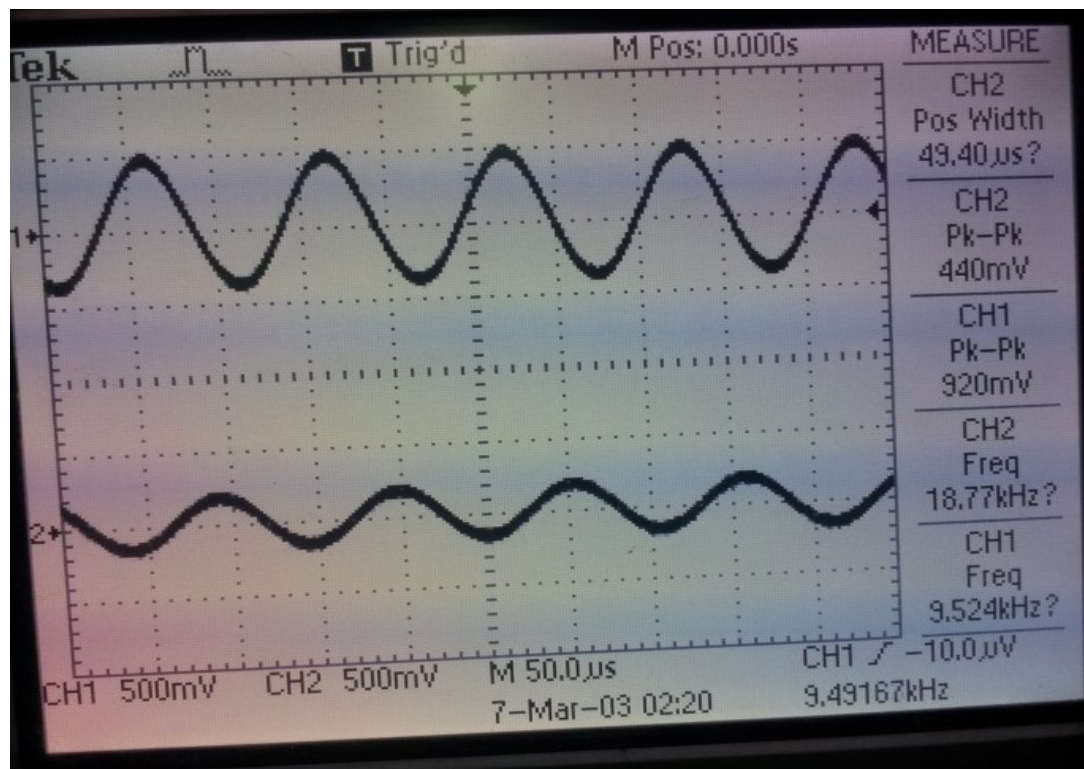

*At lower Frequency (High Pass Filter)*

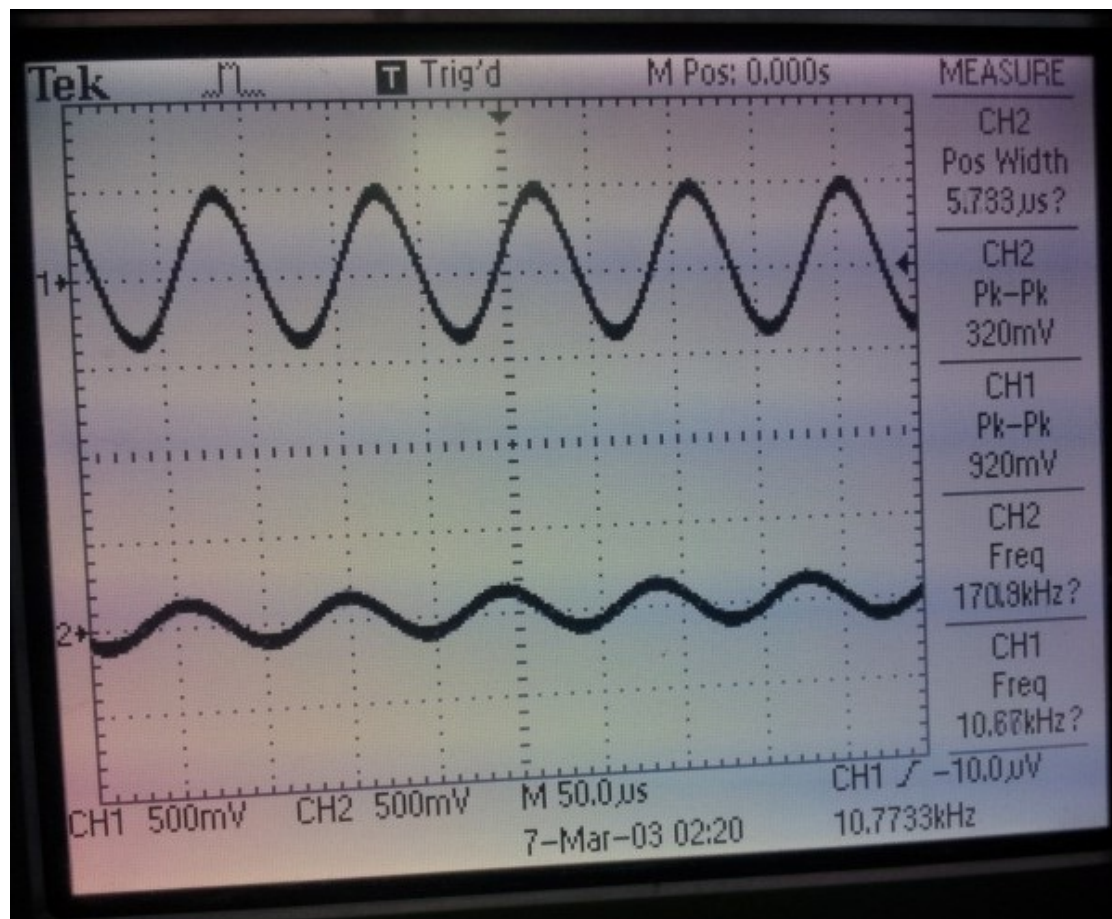

*At Higher Frequency (Low Pass Filter)*

### Our Results for Part II

With the switched capacitor our  $F_o = 9.9 \text{ kHz}$ .  $BW = 1.3 \text{ K} \rightarrow Q = 7.6$

This is because the impedance of the switched capacitor was much lower than the  $R_g$ .

## *Conclusion*

Overall, after completing our project in Electronics II (ELE341), we were able to utilize Pspice programming to analyze and design electronic circuits. Moreover, we also were able to design several circuits such as “Switched Capacitor Active Band-pass Filter” circuit where through each part of this project, we implemented one part of the whole project circuit, and we verified our results by Mr. Madathumpadical Narayanan, our Electronics II Lab instructor. Furthermore, in this project, we applied the team skills where we divided the work between ourselves in order to do the required task in less possible time. Ultimately, this project is one of the most important applications in the electronics area where we can applied our gained skills from this project in designing and implementing any electronic circuit in the future.